

ISTANBUL TECHNICAL UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BLG 222E
COMPUTER ORGANIZATION
PROJECT REPORT

PROJECT NO : 4
PROJECT DATE : 14.07.2020
GROUP NO : 31

GROUP MEMBERS:

150180001 : MEHMET ARİF DEMİRTAŞ
150180002 : BARIŞ EMRE MİŞE
150180007 : ÖMER FARUK ÖZKAN
150180009 : ERCE CAN BEKTÜRE

SPRING 2020

Contents

FRONT COVER

CONTENTS

1	INTRODUCTION	1
2	PROJECT PARTS	1
2.1	Control Logic	1
2.1.1	Branching Logic	2
2.1.2	Mapping Logic	2
2.2	Type-1 Micro-operations	5
2.2.1	READ	5
2.2.2	MREAD	5
2.2.3	STORE	6
2.2.4	BRANCH	6
2.2.5	FLAG	6
2.2.6	SETSTACK & GETSTACK	8
2.2.7	ALUA Operations: MOVN, NOTN, LSLN, LSRN	8
2.2.8	ALUAB Operations: ADDN, SUBN, ANDN, ORN	9
2.2.9	INCR & DECR	10
2.2.10	CHNGSTACK & STRSTACK	11
2.2.11	PCTIRH & PCTIRL	12
2.3	Type-2 Micro-operations	12
2.3.1	INCPC & INCSTACK & DECSTACK	12
3	RESULT	13
3.1	Operations	14
3.2	Subroutines	16
3.2.1	FETCH	16
3.2.2	DIRECT	16
3.3	The Complete Microprogram	16
4	DISCUSSION	17
5	CONCLUSION	17

1 INTRODUCTION

In this fourth project, we implemented a software-based control unit for our ALU and register system from the second project. This design has 19 operations that are specified in the project PDF, and it has access to four numbered registers R_0, R_1, R_2, R_3 and registers SP, AR, PC . We also use 16 bit instructions register IR .

We used 24 micro-operations to realize these operations in our control unit, a ROM with 19-bit data and 8-bit address, with a total of 256 addresses, with three branching conditions and four branching types.

File name is as follows:

- **hw4.circ**

Also, these files are included from the first and second project:

- **hw2part2.circ**
- **hw2part1.circ**
- **hw1part1_8.circ**
- **hw1part2a.circ**
- **hw1part2b.circ**
- **hw1part2c.circ**

2 PROJECT PARTS

2.1 Control Logic

Our initial parts are similar in design, we divide the instruction into meaningful parts such as OPCODE, REGSEL and such. But we are using software-based control in this design, as opposed to the hardwired control of the previous project.

This means that instead of hard-coding the control signals for operations themselves, we sent control signals for micro-operations. Micro-operations are simple commands that are done in a single clock cycle. Since they take single clock, we do not need a sequence counter.

We implemented 24 micro-operations in total, and we divided them into 2 categories. There are 21 type-1 micro-operations, so we denote them with a 5-bit code. Most of our micro-operations are in this category. There are 3 type-2 instructions, so we denote them

with 2 bits. The micro-operations in this category are simpler and used with some of our other micro-operations simultaneously.

We used these micro-operations as building blocks in writing micro-instructions. Each micro-instruction of ours are 19-bit. The control word, which determines the control signals for the required micro-instructions, are 7-bit, as we have a 5-bit and a 2-bit category for micro-operations. Remaining 12-bit space is made of 2-bit CD: condition for branching, 2-bit BR: type of branching, and the 8-bit address. We decide where to go next in our control memory based on this 12-bit sequencing word.

Our micro-instructions make up the micro-program, which contains all the code for different operations. Micro-program is inside the Control Memory, which is a ROM with data width 19 and address width 8, which makes this a ROM with 256 address cells. Our address is held in a 8-bit register called CAR.

2.1.1 Branching Logic

We have 3 conditions for branching, unconditional branch (which is a condition that is always true), addressing mode branching, and zero flag branching. If condition is false, we move on to the next address in the control memory. If condition is true, we do the desired type of branching.

There are 4 branching types, which are JMP, CALL, RET and MAP. JMP jumps into the specified address. CALL also goes to the address, but it also stores the next address in subroutine register SBR. RET returns us to the address hold in the SBR. These two types can be used to emulate function calls. Finally, MAP does the mapping to find the correct address to go.

CD	Condition	Symbol	BR	Branch
00	Unconditional	U	00	JMP
01	Addressing Mode	I	01	CALL
10	Zero flag	Z	10	RET
11	Unconditional	U	11	MAP

Table 1: Branching logic and types

2.1.2 Mapping Logic

Since we have a 256-bit ROM, it has 8-bit addresses. Since our OPCODEs are 5-bit, we put two zeroes in the right and a one in the left. So our OPCODEs become addresses that start at 128(hex 80) and each opcode have 4 lines until the next opcodes. First 128 bits of the control memory are reserved for subroutines.

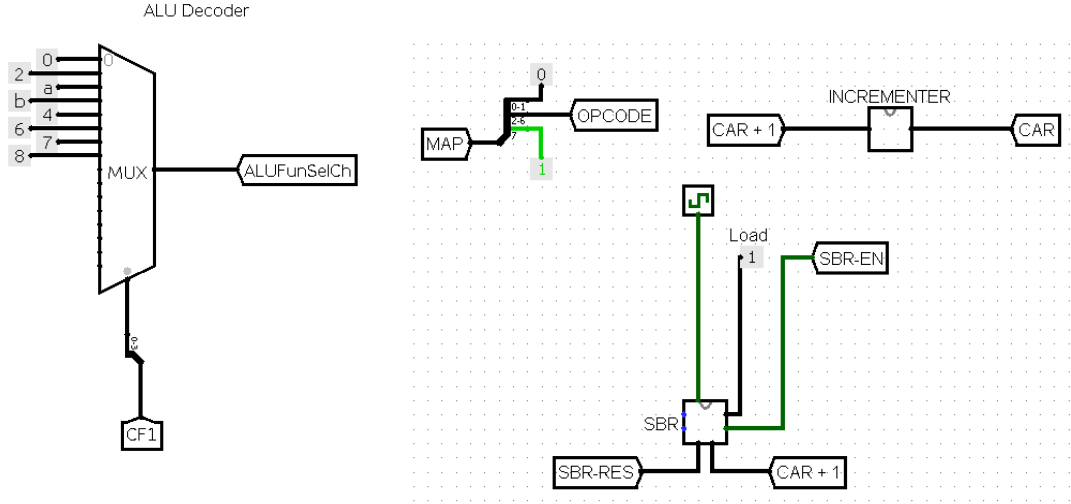


Figure 3: ALU Decoder, Mapping Logic, Incrementer, Subroutine Register

ALU Decoder is used to have multiple ALU microoperations that uses the same control signal. It will be explained in ALUA and ALUAB subsections.

μ -op	Code				
NOP	00000				
READ	00001				
MREAD	00010	μ -op	Code		
STORE	00011	MOVM	10000		
BRANCH	00100	NOTM	10001	μ -op	Code
FLAG	00101	LSLM	10010	NOP	00
SETSTACK	00110	LSRM	10011	INCPC	01
INCR	01001	ADDM	10100	INCSTACK	10
DECR	01010	SUBM	10100	DECSTACK	11
GETSTACK	01011	ANDM	10101		
CHNGSTACK	01100	ORM	10110		
STRSTACK	01101				
PCTIRH	01110				
PCTIRL	01111				

Table 2: Our microoperations for type-1(5-bit) and type-2(2-bit)

2.2 Type-1 Micro-operations

2.2.1 READ

This micro-operation reads the instructions rightmost 8-bits from instruction register into the register in part2a $Rx \leftarrow IR(0-7)$. The required register is selected by REGSEL.

 


Figure 4: Circuit of READ micro-operation

2.2.2 MREAD

This micro operation is used for direct addressing, and it reads from memory to IR, from $M[AR]$ to $IR(0-7)$. For this micro-op we need to access the memory and get output of it therefore we set ldMEM and selMEM to 1.

 


Figure 5: Circuit of MREAD micro-operation

2.2.3 STORE

In this micro-operation we read the value in Rx to $M[AR]$. For this one we need to access the memory but since we read input to the memory this time instead of ldMEM we set strMEM to 1.

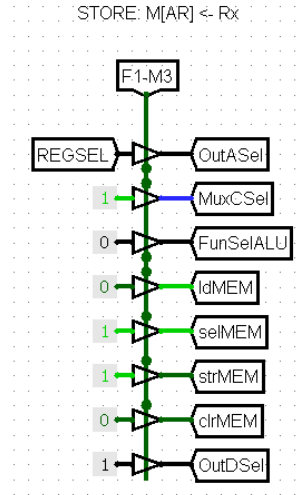


Figure 6: Circuit of STORE micro-operation

2.2.4 BRANCH

This is a rather short micro-operation, in this one we simply read the value into the PC register. Since this is an immediate operation we do not need to access the memory.

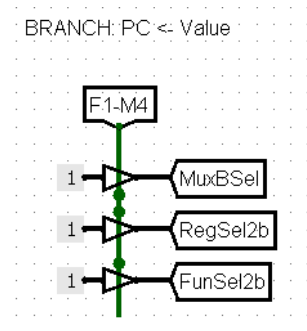


Figure 7: Circuit of BRANCH micro-operation

2.2.5 FLAG

This micro operation is designed to check the zero and negative flags. This is done by running the value through the ALU. This micro-operation is only used in increment and decrement instructions.

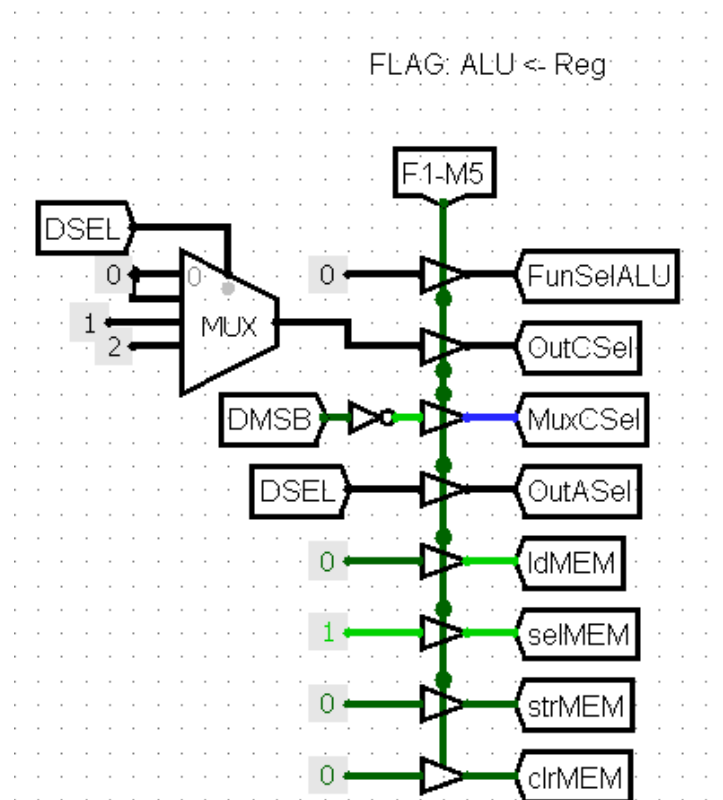


Figure 8: Circuit of FLAG micro-operation

2.2.6 SETSTACK & GETSTACK

These micro operations are opposites of each other. SETSTACK is $M[SP] \leftarrow PC$ and GETSTACK is $PC \leftarrow M[SP]$. These micro-operations are used in CAL(setstack) and RET (getstack) instructions. We store the current value of PC to the stack, we go to a subroutine and we return with RET, reading the top of the stack to PC.

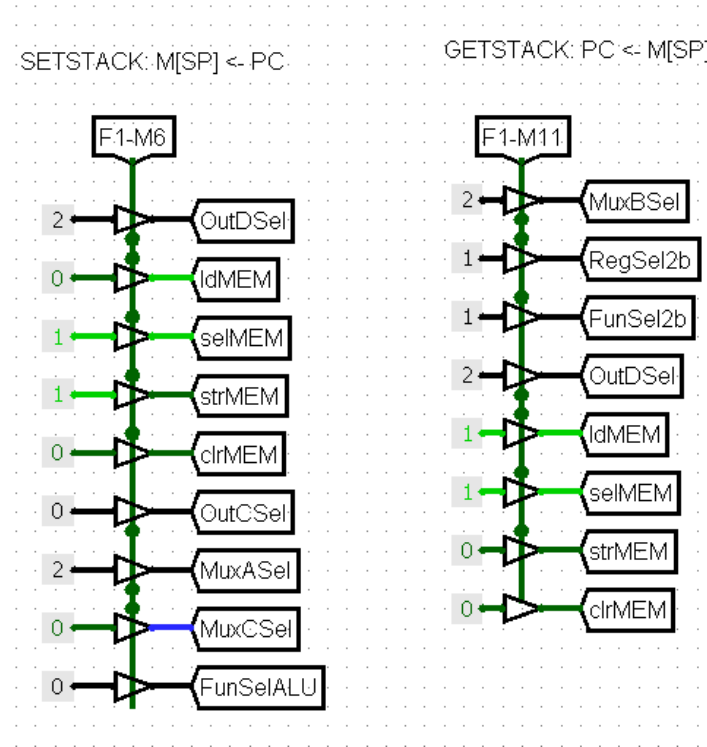


Figure 9: Circuits of SETSTACK and GETSTACK micro-operations

2.2.7 ALUA Operations: MOV, NOT, LSL, LSR

This micro-operation is used for basic ALU operations like LSL, LSR, NOT and another operation MOV. In this micro-operation we have 4 different moving states. These states are decided according to the DMSB and 1MSB, which are MSB of DESTREG and MSB of SRCREG1. The ALU operations are decided by the ALUFunSelCh, which is connected to a decoder which checks for which micro operation we selected. Our circuit takes a register, goes through the ALU and writes it into a third register, and what ALU does is determined by the ALUFunSelCh.

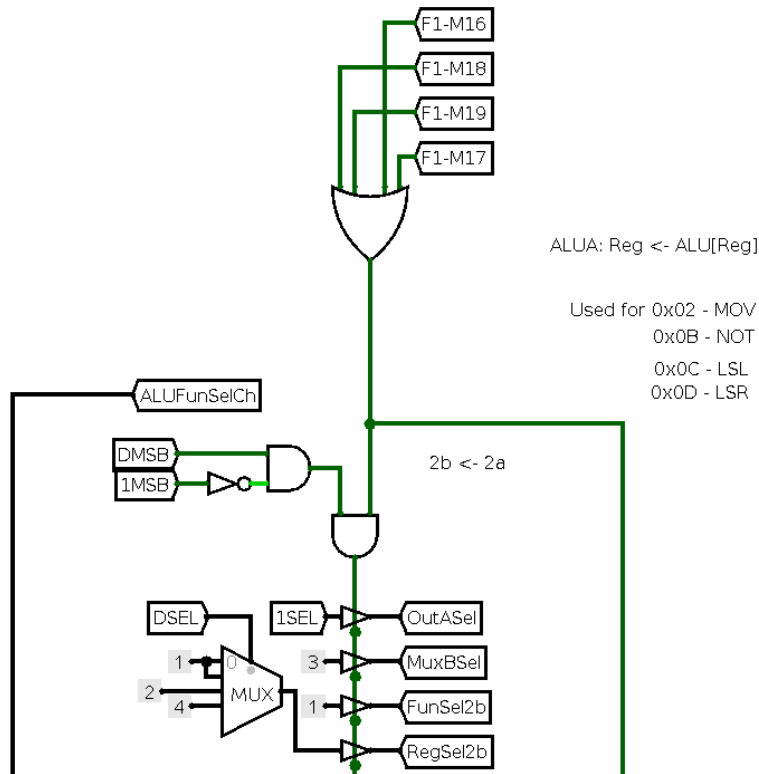


Figure 10: Circuit of ALUA micro-operations

2.2.8 ALUAB Operations: ADDM, SUBM, ANDM, ORM

In this micro operation we do the simple ALU operations with two operands like ADD, SUB, OR, AND. Just like in ALUA we have 4 different moving states for the output. To decide which operation we are doing we check ALUFunSelCh and to decide where we want to move the output we check 2MSB, 1MSB and DMSB.

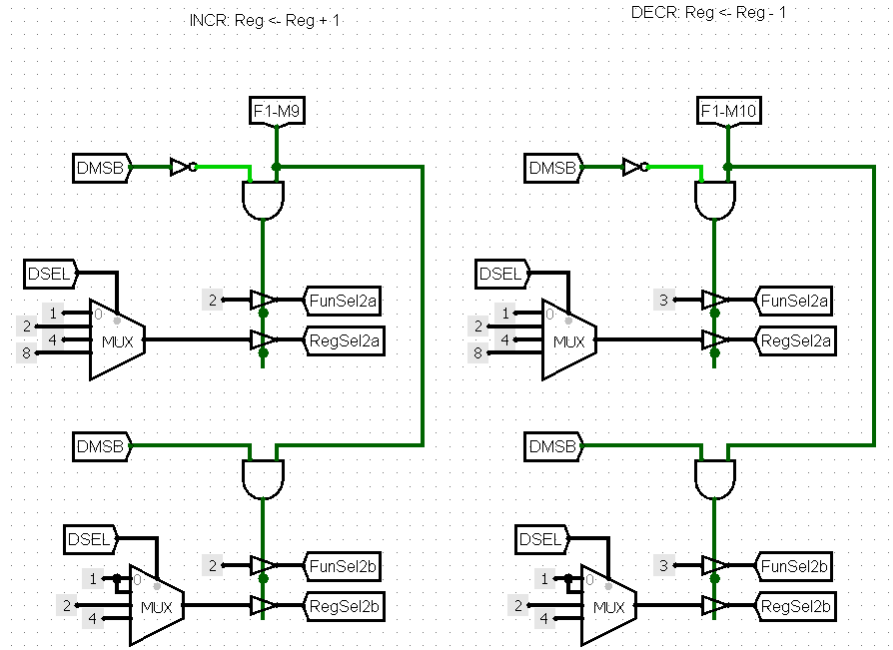


Figure 12: Circuits of INCR and DECR micro-operations

2.2.10 CHNGSTACK & STRSTACK

These micro-operations are used in PSH and PUL instructions which lets us push values to stack from registers in part2a or read values from stack to the registers in part2a.

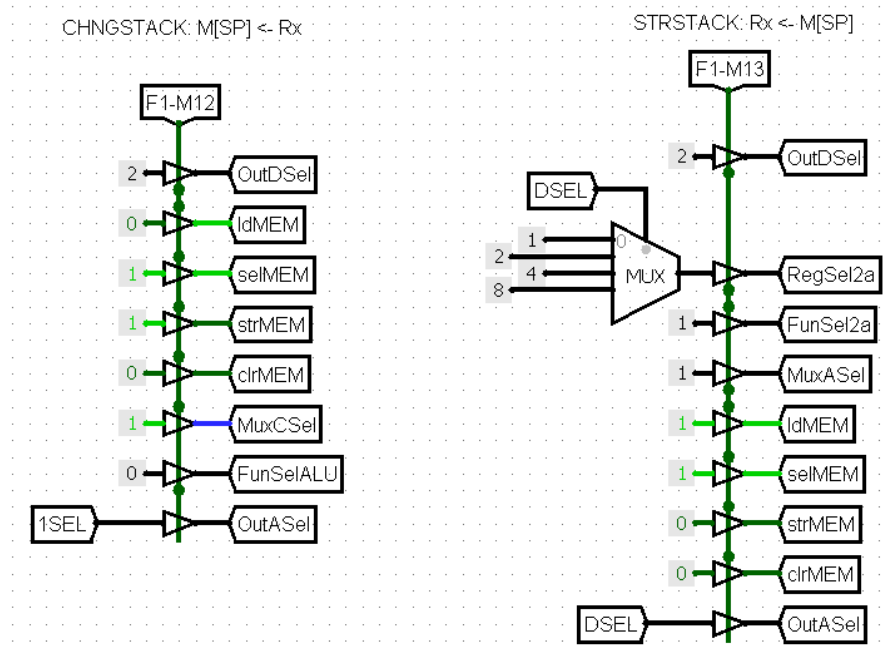


Figure 13: Circuits of CHNGSTACK and STRSTACK micro-operations

2.2.11 PCTIRH & PCTIRL

These micro-operations are used in fetch cycle. In these micro-ops we simply write the instructions from program counter (PC) into the instruction register.

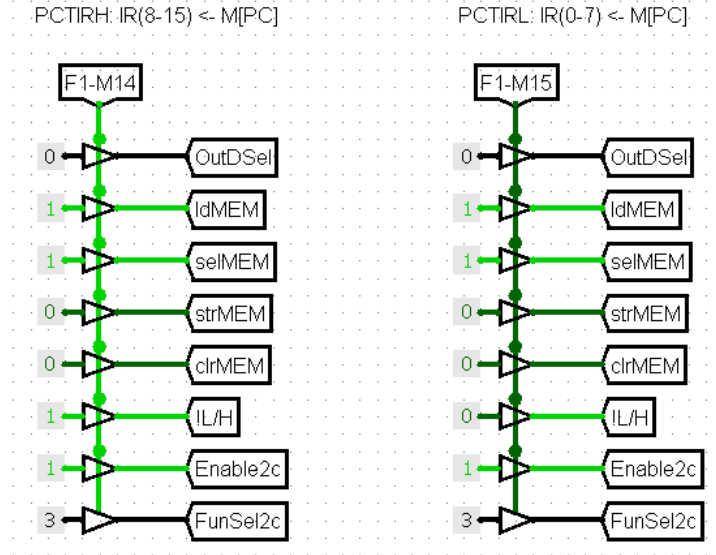


Figure 14: Circuits of PCTIRH and PCTIRL micro-operations

2.3 Type-2 Micro-operations

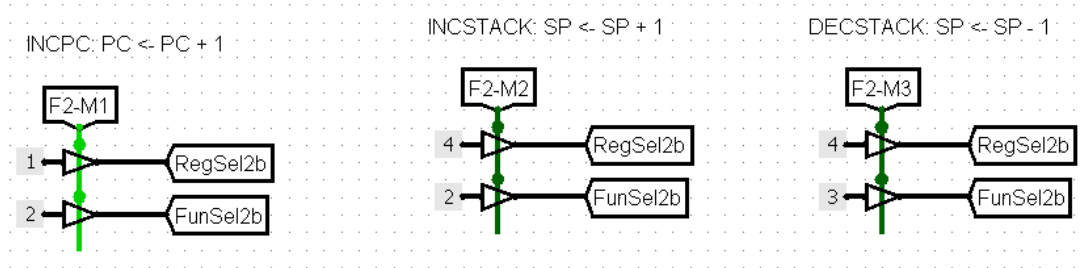


Figure 15: Circuits of INCPC, INCSTACK and DECSTACK micro-operations

2.3.1 INCPC & INCSTACK & DECSTACK

These micro-operations are Type-2 (F2) Micro-operations because some of these micro-operations' registers clash therefore they can not be Type-1. INCSTACK and DECSTACK operations are used in PSH and PUL instructions. When pushing to the stack we use DECSTACK and when pulling out of the stack we use INCSTACK. We use INCPC to jump to the next instruction in the fetch cycle.

3 RESULT

The following are our test cases from the third project. They still work without any problem.

Our first test case is the example program from PDF, which sums up from M[A0] to M[A4] and writes the output to M[A6]. PDF says result is written to M[A5], but to do this, we should delete the increment line, which is the instructions before the last one.

Listing 1: Example code in human readable form.

```
1 BRA PC IM 0x20
2 SKIP 15
3 LD R0 IM 0x05
4 LD R1 IM 0x00
5 LD R2 IM 0xA0
6 MOV AR R2
7 LD R2 D 0x00
8 INC AR AR
9 ADD R1 R1 R2
10 DEC R0 R0
11 BNE PC IM 0x28
12 INC AR AR
13 ST R1 D 0x00
```

Listing 2: Example code in hex logisim memory image form.

```
1 v2.0 raw
2 70 20 30*00 00 05 02 00 04 a0 16 40 05 00 46 c0 29 28 38 00 80 28 46 c0 0b 00
```

Our test case for bonus points, which subtracts R1 value from AR value and writes it to R3.

Listing 3: Example code in human readable form.

```
1 LD R0 IM 0x09
2 LD R1 IM 0x03
3 MOV AR R0
4 SUB R3 AR R1
```

Listing 4: Example code in hex logisim memory image form.

```
1 v2.0 raw
```

```
2 00 09 02 03 16 00 33 c4
```

Another example code we have written writes Fibonacci sequence to memory, starting from 0x30 address.

Listing 5: Example code in human readable form.

```
1 BRA PC D 0x10
2 SKIP 7
3 LD R0 IM 0x30
4 LD R1 IM 0x01
5 LD R2 IM 0x01
6 MOV AR R0
7 ADD R3 R1 R2
8 ST R3 D 0x00
9 INC AR AR
10 MOV R1 R2
11 MOV R2 R3
12 BRA PC D 0x18
```

Listing 6: Example code in hex logisim memory image form.

```
1 v2.0 raw
2 71 10 14*00 00 30 02 01 04 01 16 00 2b 28 0f 00 46 c0 11 40 12 60 71 18
```

3.1 Operations

We implemented all 19 operations in the following code. We start at address 128 and each operation is stored 4 addresses later.

Listing 7: Machine code for operations.

```
1 ORG 128
2 LOAD: NOP I CALL DIRECT
3       READ U JMP FETCH
4 ORG 132
5 STORE: STORE U JMP FETCH
6 ORG 136
7 MV: MOVM U JMP FETCH
8 ORG 140
9 PSH: CHNGSTACK U JMP NEXT
10      DECSTACK U JMP FETCH
```



```

11  ORG 144
12  PUL: INCSTACK U JMP NEXT
13      STRSTACK U JMP FETCH
14  ORG 148
15  ADD: ADDM U JMP FETCH
16  ORG 152
17  SUB: SUBM U JMP FETCH
18  ORG 156
19  DEC: DECR U JMP NEXT
20      FLAG U JMP FETCH
21  ORG 160
22  INC: INCR U JMP NEXT
23      FLAG U JMP FETCH
24  ORG 164
25  AND: ANDM U JMP FETCH
26  ORG 168
27  OR: ORM U JMP FETCH
28  ORG 172
29  NOT: NOTM U JMP FETCH
30  ORG 176
31  LSL: LSLM U JMP FETCH
32  ORG 180
33  LSR: LSRM U JMP FETCH
34  ORG 184
35  BRA: BRANCH U JMP FETCH
36  ORG 188
37  BEQ: NOP Z JMP BRA
38      NOP U JMP FETCH
39  ORG 192
40  BNE: NOP Z JMP FETCH
41      NOP U JMP BRA
42  ORG 196
43  CALL: SETSTACK, DECSTACK U JMP NEXT
44      BRANCH U JMP FETCH
45  ORG 200
46  RET: NOP, INCSTACK U JMP NEXT
47      GETSTACK U JMP FETCH

```

3.2 Subroutines

We implemented 2 subroutines, FETCH and DIRECT.

Listing 8: Subroutine declarations in machine code.

```
1  ORG 0
2  FETCH: PCTIRH, INCPC U JMP NEXT
3          PCTIRL, INCPC U MAP EMPTY
4  ORG 4
5  DIRECT: MREAD U RET EMPTY
```

3.2.1 FETCH

FETCH subroutine takes two lines of micro-instructions and uses PCTIRL, PCTIRH and INCPC to fetch an instruction from the computer memory (RAM) and MAP to the corresponding OP CODE.

3.2.2 DIRECT

DIRECT subroutine uses MREAD micro-operation to read the direct value into the IR so in other micro-operations we can use it as an immediate value such as the LOAD operation.

3.3 The Complete Microprogram

Listing 9: The hex file for the whole microprogram.

```
1  v2.0 raw
2  39001 3d302 00000 00000 08205 00000 00000 00000 00000 00000 00000 00000 00000
    00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000
    00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000
    00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000
    00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000
    00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000
    00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000 00000
    00000 00000 00000 00000 00000 00000 00000 00504 04000 00000 00000 0c000
    00000 00000 00000 40000 00000 00000 00000 3008d 00000 00000 00000 00091
    34000 00000 00000 50000 00000 00000 00000 54000 00000 00000 00000 2809d
```

```
14000 00000 00000 240a1 14000 00000 00000 58000 00000 00000 00000 5c000
00000 00000 00000 44000 00000 00000 00000 48000 00000 00000 00000 4c000
00000 00000 00000 10000 00000 00000 00000 008b8 00000 00000 00000 00800
000b8 00000 00000 1b0c5 10000 00000 00000 020c9 2c000
```

4 DISCUSSION

In this project, we completely implemented a basic CPU with software-based (micro-programmed) control unit. This project was mainly on control unit and control memory, and we used different Logisim gates and units together. We learned using tunnels to represent connections, and this project would be a lot more chaotic without tunnel usage and ROM usage. We also heavily used controlled buffers as we did in the third project. This was another big organisation and we designed it more carefully. Designing micro operations was easy but we spent time creating a well-crafted micro program, watching out for edge cases in programming. We believe we avoided such errors.

5 CONCLUSION

In conclusion of this project we have learned a lot about software side of a basic computer by implementing lots and lots of instructions on Logisim and gained many information about basic central processing units.